

# LABORATORIO N° 1

*Diseño Digital Avanzado*

Mathias Sebastian Garcia

29 de septiembre de 2024

# Índice

<b>1. Código RTL</b>	<b>2</b>
1.1. Contador . . . . .	2
1.2. Shift register . . . . .	4
1.3. Top . . . . .	5
<b>2. Testbench</b>	<b>7</b>
2.1. Código . . . . .	7
2.2. Capturas de simulación . . . . .	10
<b>3. Implementación en FPGA</b>	<b>11</b>
3.1. Wrapper VIO . . . . .	11
3.2. Wrapper ILA . . . . .	12
3.3. Wrapper completo . . . . .	13
3.4. Capturas . . . . .	15

# 1. Código RTL

[Link de github](#) a los archivos de RTL.

## 1.1. Contador

```
module counter
#(
    // * -----
    // * Parameters
    // * -----
    parameter          NB_COUNTER    = 32          ,
    parameter          NB_SW         = 3           ,
    parameter          ADD_PIPE_OUT  = 0           ,
)
(
    // * -----
    // * Outputs
    // * -----
    output logic       o_count_reached              ,

    // * -----
    // * Inputs
    // * -----
    input logic [ NB_SW - 1 : 0 ] i_sw              ,

    // * -----
    // * Clock and reset
    // * -----
    input logic         i_reset                     ,
    input logic         i_clock                     ,
);
    // * -----
    // * Localparams
    // * -----
    localparam         R0            = 2**(NB_COUNTER-10)-1 ;
    localparam         R1            = 2**(NB_COUNTER-11)-1 ;
    localparam         R2            = 2**(NB_COUNTER-12)-1 ;
    localparam         R3            = 2**(NB_COUNTER-13)-1 ;

    // * -----
    // * Internal logics
    // * -----
    logic [ NB_COUNTER - 1 : 0 ] count              ;
    logic [ NB_COUNTER - 1 : 0 ] next_count          ;
    logic [ NB_COUNTER - 1 : 0 ] limit_count         ;
    logic limit_reached                             ;
    logic count_enable                               ;
    logic piped_limit_reached                       ;

    // * -----
    // * Max count decode
    // * -----
    always_comb
    begin : proc_limit_count_decode
        unique case (i_sw[2:1]) inside
            2'b00: limit_count = R0[NB_COUNTER-1:0];
            2'b01: limit_count = R1[NB_COUNTER-1:0];
            2'b10: limit_count = R2[NB_COUNTER-1:0];
            2'b11: limit_count = R3[NB_COUNTER-1:0];
        endcase
    end

    // * -----
    // * Count process
    // * -----
    assign next_count    = count + {{NB_COUNTER-1{1'b0}}, 1'b1} ;
    assign count_enable  = i_sw[0] ;
    assign limit_reached = (count >= limit_count) && count_enable ;

    always_ff @(posedge i_clock)
    begin : proc_count
        if (i_reset || limit_reached)
            count <= '0;
        else if (count_enable)
            count <= next_count;
    end

    // * -----
    // * Piping output
```

```

// * -----
generate
  if (ADD_PIPE_OUT)
    begin : gen_out_piped
      always_ff @(posedge i_clock)
        begin : proc_pipe_out
          piped_limit_reached <= limit_reached;
        end
      end else
        begin : gen_out_unpiped
          assign piped_limit_reached = limit_reached;
        end
      end
    endgenerate

// * -----
// * Output assignment
// * -----
assign o_count_reached = piped_limit_reached;
endmodule

```

## 1.2. Shift register

```
module shiftreg
#(
    // * -----
    // * Parameters
    // * -----
    parameter                NB_DATA    = 3
)
(
    // * -----
    // * Outputs
    // * -----
    output logic [ NB_DATA - 1 : 0 ] o_led        ,

    // * -----
    // * Inputs
    // * -----
    input  logic                i_valid        ,

    // * -----
    // * Clock and reset
    // * -----
    input  logic                i_reset        ,
    input  logic                i_clock
);
    // * -----
    // * Internal logics
    // * -----
    logic                [ NB_DATA - 1 : 0 ] shift_register ;

    // * -----
    // * Shift register
    // * -----
    always_ff @(posedge i_clock)
    begin : proc_data_move
        if (i_reset)
            shift_register <= {{NB_DATA-1{1'b0}}, 1'b1};
        else if (i_valid)
            shift_register <= {shift_register[NB_DATA-2:0], shift_register[NB_DATA-1]};
    end

    // * -----
    // * Output assignment
    // * -----
    assign o_led = shift_register;
endmodule
```

### 1.3. Top

```

module shiftleds
#(
    // * -----
    // * Parameters
    // * -----
    parameter          N_LEDS      = 4      ,
    parameter          NB_COUNTER = 32      ,
    parameter          NB_SW       = 4
)
(
    // * -----
    // * Outputs
    // * -----
    output logic [ N_LEDS - 1 : 0 ] o_led      ,
    output logic [ N_LEDS - 1 : 0 ] o_led_b    ,
    output logic [ N_LEDS - 1 : 0 ] o_led_g    ,

    // * -----
    // * Inputs
    // * -----
    input  logic [ NB_SW - 1 : 0 ] i_sw      ,

    // * -----
    // * Clock and reset
    // * -----
    input  logic          i_reset      ,
    input  logic          i_clock
);

// * -----
// * Internal logics
// * -----
logic          counter_count_reached ;
logic [ N_LEDS - 1 : 0 ] shiftreg_led ;

// * -----
// * Counter instantiation
// * -----
counter
#(
    .NB_COUNTER ( NB_COUNTER      ) ,
    .NB_SW      ( NB_SW - 1      )
)
u_counter
(
    .o_count_reached ( counter_count_reached ) ,
    .i_sw            ( i_sw [NB_SW-2:0] ) ,
    .i_reset         ( ~i_reset      ) ,
    .i_clock         ( i_clock       )
);

// * -----
// * Shift register instantiation
// * -----
shiftreg
#(
    .NB_DATA      ( N_LEDS      )
)
u_shiftreg
(
    .o_led      ( shiftreg_led      ) ,
    .i_valid    ( counter_count_reached ) ,
    .i_reset    ( ~i_reset      ) ,
    .i_clock    ( i_clock       )
);

// * -----
// * Output assignment
// * -----
assign o_led      = shiftreg_led ;
assign o_led_b = (i_sw[3]) ? shiftreg_led : '0 ;
assign o_led_g = (i_sw[3]) ? '0 : shiftreg_led ;

// * -----
// * Assertions
// * -----
`ifdef ENABLE_SVA
    logic enable_sva = 1'b1;

    assert property (

```

```

        @(posedge i_clock)
        disable iff (!enable_sva)
        counter_count_reached | => !counter_count_reached
    ) else $error("Valid signal for shift register lasted more than one clock");

    assert property (
        @(posedge i_clock)
        disable iff (!enable_sva)
        $rose(counter_count_reached) | => (u_counter.count == 0)
    ) else $error("Counter limit reached but count register didnt go back to zero. Count value: %0d", u_counter.count);

    assert property (
        @(posedge i_clock)
        disable iff (!enable_sva)
        (u_counter.count == u_counter.limit_count) | -> $rose(counter_count_reached)
    ) else $error("Limit count reached but count reached never rose");

    assert property (
        @(posedge i_clock)
        disable iff (!enable_sva)
        $fell(i_reset) | => (u_counter.count == 0)
    ) else $error("Reset negedge happened but counter didnt set to default value. Count value: %0d", u_counter.count);

    assert property (
        @(posedge i_clock)
        disable iff (!enable_sva)
        $fell(i_reset) | => (u_shiftreg.shift_register == {{N_LEDS-1{1'b0}}, 1'b1})
    ) else $error("Reset negedge happened but shift register didnt set to default value. Value found: %0b", u_shiftreg.shift_register);

    assert property (
        @(posedge i_clock)
        disable iff (!enable_sva)
        !i_sw[0] | => $stable(u_counter.count)
    ) else $error("Count is not stable during disable");
`endif
endmodule

```

## 2. Testbench

[Link de github](#) al archivo de testbench.

### 2.1. Código

```
`timescale 1ns/100ps

`define N_LEDS      4
`define NB_SEL      2
`define NB_COUNTER  32
`define NB_SW       4
`define CLOCK_PERIOD_NS 10

module tb_shiftleds();
    // * -----
    // * Localparams
    // * -----
    localparam          N_LEDS      = `N_LEDS      ;
    localparam          NB_SEL      = `NB_SEL      ;
    localparam          NB_COUNTER  = `NB_COUNTER  ;
    localparam          NB_SW       = `NB_SW       ;

    // * -----
    // * Declaration
    // * -----
    wire [ N_LEDS      - 1 : 0 ] o_led          ;
    wire [ N_LEDS      - 1 : 0 ] o_led_b        ;
    wire [ N_LEDS      - 1 : 0 ] o_led_g        ;
    reg  [ NB_SW       - 1 : 0 ] i_sw           ;
    reg                                i_reset      ;
    reg                                i_clock       ;

    wire [ NB_COUNTER - 1 : 0 ] active_count_limit ;
    wire [ NB_COUNTER - 1 : 0 ] counter_limit [4]  ;

    reg  [ NB_COUNTER - 1 : 0 ] counter_record    ;

    // * -----
    // * Observers assigns
    // * -----
    assign counter_limit[0] = u_shiftleds.u_counter.R0;
    assign counter_limit[1] = u_shiftleds.u_counter.R1;
    assign counter_limit[2] = u_shiftleds.u_counter.R2;
    assign counter_limit[3] = u_shiftleds.u_counter.R3;

    assign active_count_limit = (i_sw[2:1] == 2'b00 ) ? counter_limit[0] :
                                (i_sw[2:1] == 2'b01 ) ? counter_limit[1] :
                                (i_sw[2:1] == 2'b10 ) ? counter_limit[2] :
                                counter_limit[3] ;

    // * -----
    // * Clock generation
    // * -----
    initial
    begin : proc_clock_initializacion
        i_clock = '0;
    end
    always #(`CLOCK_PERIOD_NS/2) i_clock = ~i_clock;

    // * -----
    // * Tasks
    // * -----
    task automatic wait_for_n_clocks(int n_clocks = 1, bit safe_check = 1'b1);
        repeat(n_clocks) @(posedge i_clock);
        if (safe_check) #1ns;
    endtask : wait_for_n_clocks

    task automatic run_reset(int clock_duration = 1);
        wait_for_n_clocks(.n_clocks(1), .safe_check(0));
        force i_reset = 1'b0;
        wait_for_n_clocks(.n_clocks(clock_duration), .safe_check(0));
        force i_reset = 1'b1;
    endtask : run_reset

    task automatic check_led_change(int n_changes = N_LEDS);
        logic [N_LEDS-1:0] led_record;
        repeat (n_changes) begin : proc_check_repeatedly
            led_record = u_shiftleds.o_led;
            wait_for_n_clocks(active_count_limit);
        end
    endtask : check_led_change
```



```

        assert(u_shiftleds.counter_count_reached == 1'b1);
        wait_for_n_clocks(1);
        assert(o_led == {led_record[N_LEDS-2:0], led_record[N_LEDS-1]});
        if (i_sw[3]) begin
            assert (o_led_b == o_led);
            assert (o_led_g == '0 );
        end else begin
            assert (o_led_b == '0 );
            assert (o_led_g == o_led);
        end
        $display("Led value: %4b - Led recorded: %4b - Expected value: %4b", o_led, led_record, {led_record[N_LEDS-2:0], led_record[N_LEDS-1]});
    end
endtask : check_led_change

// * -----
// * Assertion handling
// * -----
initial
begin : proc_bypass_sva_first_clock
    $assertoff(0,u_shiftleds);
    wait_for_n_clocks(.n_clocks(2), .safe_check(0));
    $asserton(0,u_shiftleds);
end

// * -----
// * Stimulus generation
// * -----
initial
begin : proc_stimulus
    i_sw = '0;
    i_reset = 1'b0;
    run_reset(5);
    wait_for_n_clocks(20);

    i_sw[0] = 1'b1;
    check_led_change(8);
    wait_for_n_clocks(4);

    i_sw[2:1] = 2'b01;
    run_reset();
    check_led_change(8);

    i_sw[3] = 1'b1 ;
    i_sw[2:1] = 2'b10;
    run_reset();
    check_led_change(8);

    i_sw[2:1] = 2'b11;
    run_reset();
    check_led_change(8);

    wait_for_n_clocks(.n_clocks(100), .safe_check(0));
    i_sw[0] = 1'b0;
    wait_for_n_clocks(.n_clocks(2000), .safe_check(0));

    counter_record = u_shiftleds.u_counter.count;
    i_sw[0] = 1'b1;
    wait_for_n_clocks(1);
    assert(u_shiftleds.u_counter.count == counter_record+1);

    $finish;
end

// * -----
// * DUT instantiation
// * -----
shiftleds
#(
    .N_LEDS      ( N_LEDS      ),
    .NB_COUNTER  ( NB_COUNTER ),
    .NB_SW       ( NB_SW       )
)
u_shiftleds
(
    .o_led      ( o_led      ),
    .o_led_b    ( o_led_b    ),
    .o_led_g    ( o_led_g    ),
    .i_sw       ( i_sw       ),
    .i_reset    ( i_reset    ),
    .i_clock    ( i_clock    )
);

```

```
endmodule
```

## 2.2. Capturas de simulación

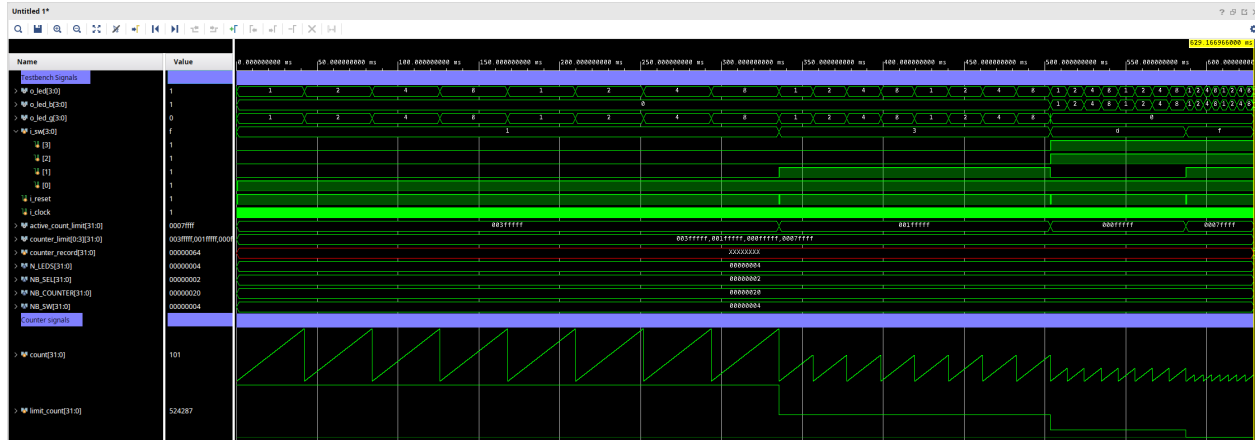


Figura 1: Operación normal

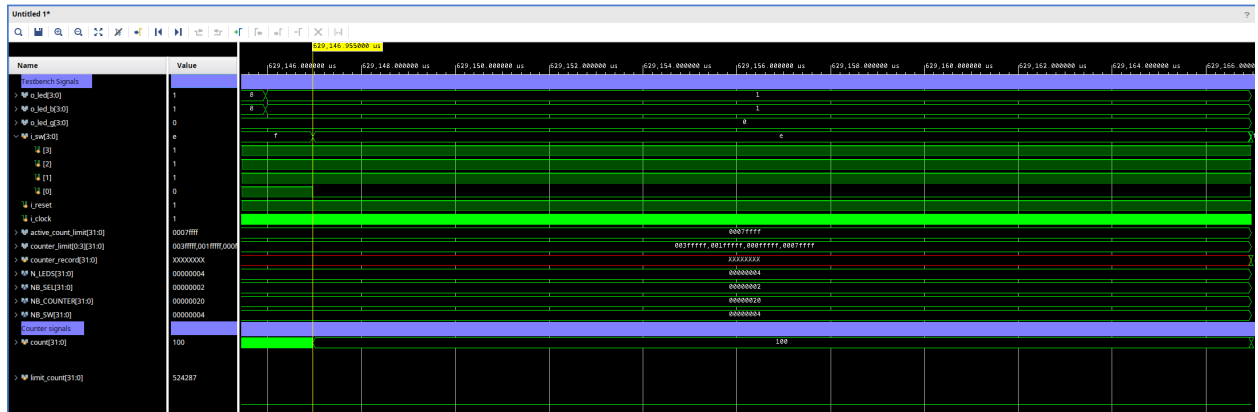


Figura 2:  $sw[0] = 0$  mantiene la cuenta y los leds sin alterar

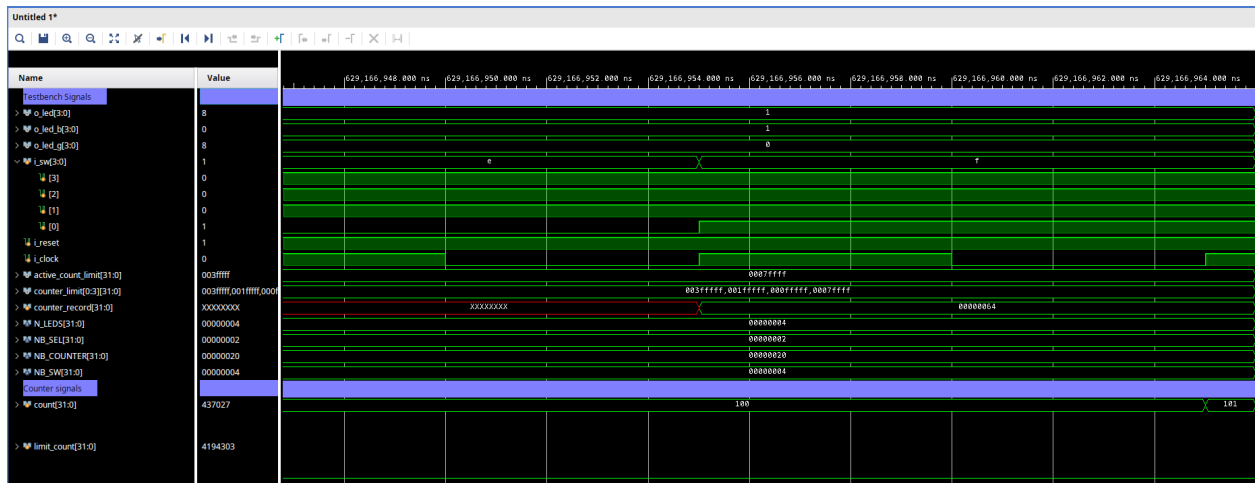


Figura 3: Volver a setear  $sw[0] = 1$  retoma la cuenta desde el valor previo

### 3. Implementación en FPGA

[Link de github](#) a los archivos de los wrappers.

#### 3.1. Wrapper VIO

```
//Copyright 1986-2022 Xilinx, Inc. All Rights Reserved.
//Copyright 2022-2023 Advanced Micro Devices, Inc. All Rights Reserved.
//-----
//Tool Version: Vivado v.2023.1 (lin64) Build 3865809 Sun May  7 15:04:56 MDT 2023
//Date       : Sat Sep 28 23:19:27 2024
//Host      : dsktp running 64-bit Fedora Linux 40 (KDE Plasma)
//Command   : generate_target vio_wrapper.bd
//Design    : vio_wrapper
//Purpose   : IP block netlist
//-----
`timescale 1 ps / 1 ps

module vio_wrapper
    (clk_0,
     probe_in0_0,
     probe_in1_0,
     probe_in2_0,
     probe_out0_0,
     probe_out1_0,
     probe_out2_0);
    input clk_0;
    input [3:0]probe_in0_0;
    input [3:0]probe_in1_0;
    input [3:0]probe_in2_0;
    output [0:0]probe_out0_0;
    output [0:0]probe_out1_0;
    output [3:0]probe_out2_0;

    wire clk_0;
    wire [3:0]probe_in0_0;
    wire [3:0]probe_in1_0;
    wire [3:0]probe_in2_0;
    wire [0:0]probe_out0_0;
    wire [0:0]probe_out1_0;
    wire [3:0]probe_out2_0;

    vio vio_i
        (.clk_0(clk_0),
         .probe_in0_0(probe_in0_0),
         .probe_in1_0(probe_in1_0),
         .probe_in2_0(probe_in2_0),
         .probe_out0_0(probe_out0_0),
         .probe_out1_0(probe_out1_0),
         .probe_out2_0(probe_out2_0));
endmodule
```

### 3.2. Wrapper ILA

```
//Copyright 1986-2022 Xilinx, Inc. All Rights Reserved.
//Copyright 2022-2023 Advanced Micro Devices, Inc. All Rights Reserved.
//-----
//Tool Version: Vivado v.2023.1 (lin64) Build 3865809 Sun May  7 15:04:56 MDT 2023
//Date       : Sat Sep 28 23:21:04 2024
//Host       : dsktp running 64-bit Fedora Linux 40 (KDE Plasma)
//Command    : generate_target ila_wrapper.bd
//Design     : ila_wrapper
//Purpose    : IP block netlist
//-----
`timescale 1 ps / 1 ps

module ila_wrapper
    (clk_0,
     probe0_0,
     probe1_0,
     probe2_0);
    input clk_0;
    input [3:0]probe0_0;
    input [3:0]probe1_0;
    input [3:0]probe2_0;

    wire clk_0;
    wire [3:0]probe0_0;
    wire [3:0]probe1_0;
    wire [3:0]probe2_0;

    ila ila_i
        (.clk_0(clk_0),
         .probe0_0(probe0_0),
         .probe1_0(probe1_0),
         .probe2_0(probe2_0));
endmodule
```

### 3.3. Wrapper completo

```

module shiftleds_wrapper (
    // * -----
    // * Outputs
    // * -----
    output logic [4-1:0] o_led      ,
    output logic [4-1:0] o_led_b    ,
    output logic [4-1:0] o_led_g    ,

    // * -----
    // * Inputs
    // * -----
    input logic  [4-1:0] i_sw        ,

    // * -----
    // * Clock and reset
    // * -----
    input logic      i_reset_n      ,
    input logic      i_clock        ,
);

// * -----
// * Internal logics
// * -----
logic      [4-1:0] shiftleds_led   ;
logic      [4-1:0] shiftleds_led_b ;
logic      [4-1:0] shiftleds_led_g ;
logic      [4-1:0] vio_sw          ;
logic      vio_reset               ;
logic      vio_enable              ;
logic      [4-1:0] sw_to_device    ;
logic      reset_to_device         ;

// * -----
// * VIO instantiation
// * -----
vio_wrapper
u_vio_wrapper
(
    .clk_0      ( i_clock          ),
    .probe_in0_0 ( shiftleds_led    ),
    .probe_in1_0 ( shiftleds_led_b  ),
    .probe_in2_0 ( shiftleds_led_g  ),
    .probe_out0_0 ( vio_enable       ),
    .probe_out1_0 ( vio_reset        ),
    .probe_out2_0 ( vio_sw           )
);

// * -----
// * ILA instantiation
// * -----
ila_wrapper
u_ila_wrapper
(
    .clk_0      ( i_clock          ),
    .probe0_0    ( shiftleds_led    ),
    .probe1_0    ( shiftleds_led_b  ),
    .probe2_0    ( shiftleds_led_g  )
);

// * -----
// * Muxing shiftleds input
// * -----
assign sw_to_device  = (vio_enable) ? vio_sw : i_sw ;
assign reset_to_device = (vio_enable) ? ~vio_reset : i_reset_n ;

// * -----
// * Main device
// * -----
shiftleds
u_shiftleds
(
    .o_led      ( shiftleds_led    ),
    .o_led_b    ( shiftleds_led_b  ),
    .o_led_g    ( shiftleds_led_g  ),
    .i_sw       ( sw_to_device     ),
    .i_reset    ( reset_to_device   ),
    .i_clock    ( i_clock          )
);

// * -----


```

```
// * Output assign
// * -----
assign o_led  = shiftleds_led  ;
assign o_led_b = shiftleds_led_b ;
assign o_led_g = shiftleds_led_g ;
endmodule
```

3.4. Capturas

hw_vio_1					
<div><div></div><div></div><div></div><div></div><div></div></div>					
Name	Value	Activity	Direction	VIO	
> u_vio_wrapper/vio_i/probe_in2_0_1[3:0]	[H] 8	<div></div>	Input	hw_vio_1	
u_vio_wrapper/vio_i/vio_0_probe_out0	[B] 1	<div></div>	Output	hw_vio_1	
u_vio_wrapper/vio_i/vio_0_probe_out1	[B] 0	<div></div>	Output	hw_vio_1	
> u_vio_wrapper/vio_i/vio_0_probe_out2[3:0]	[H] 7	<div></div>	Output	hw_vio_1	
u_vio_wrapper/vio_i/probe_in0_0_1[3:0]	[H] 8	<div></div>	Input	hw_vio_1	
u_vio_wrapper/vio_i/probe_in1_0_1[3:0]	[H] 0	<div></div>	Input	hw_vio_1	

(a) VIO

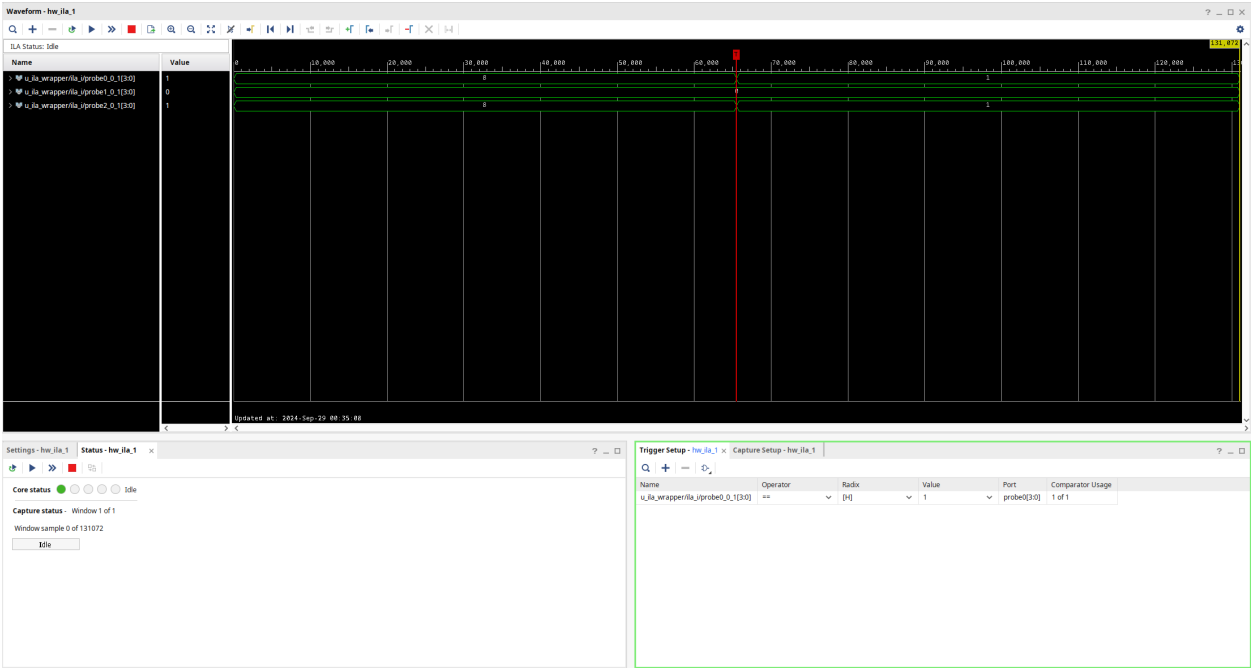


(b) ILA

Figura 4: Led verde seleccionado



hw_vio_1					
Name	Value	Activity	Direction	VIO	
> u_vio_wrapper/vio_i/probe_in2_0_1[3:0]	[H] 0		Input	hw_vio_1	
u_vio_wrapper/vio_i/vio_0_probe_out0	[B] 1		Output	hw_vio_1	
u_vio_wrapper/vio_i/vio_0_probe_out1	[B] 0		Output	hw_vio_1	
> u_vio_wrapper/vio_i/vio_0_probe_out2[3:0]	[H] F		Output	hw_vio_1	
> u_vio_wrapper/vio_i/probe_in0_0_1[3:0]	[H] 4		Input	hw_vio_1	
u_vio_wrapper/vio_i/probe_in1_0_1[3:0]	[H] 4		Input	hw_vio_1	

(a) VIO

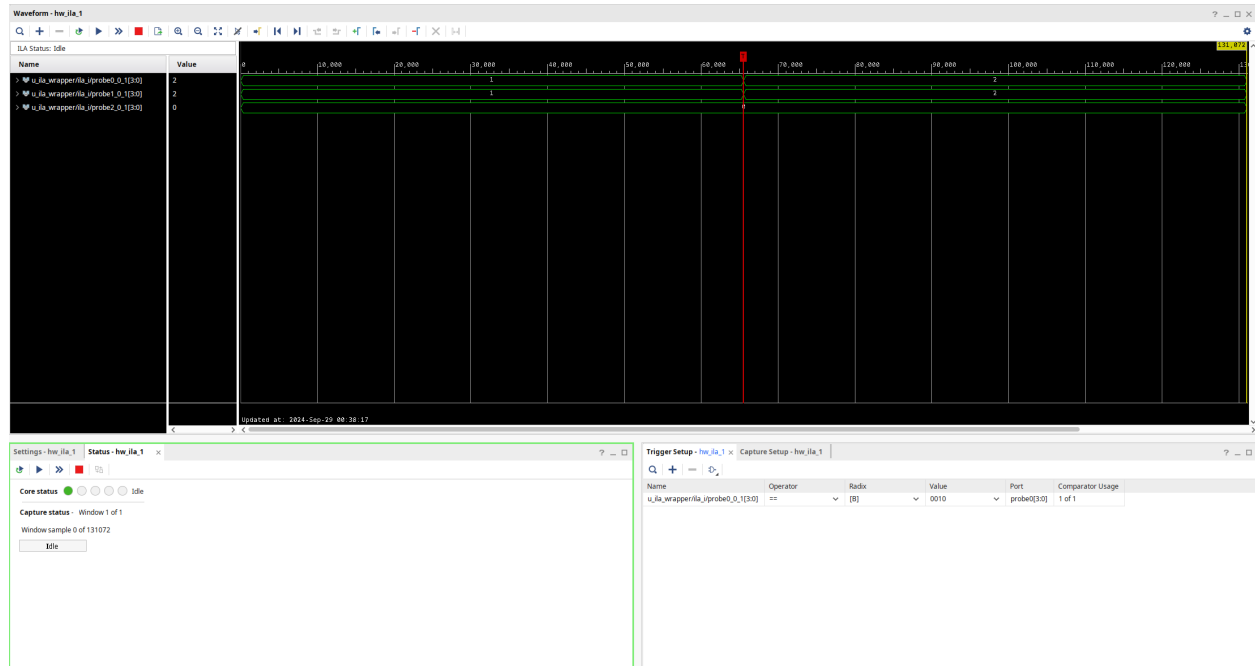


(b) ILA

Figura 5: Led azul seleccionado


hw\_vio\_1

Name	Value	Activity	Direction	VIO
u_vio_wrapper/vio_i/probe_in2_0_1[3:0]	[H] 0		Input	hw_vio_1
u_vio_wrapper/vio_i/vio_0_probe_out0	[B] 1		Output	hw_vio_1
u_vio_wrapper/vio_i/vio_0_probe_out1	[B] 0		Output	hw_vio_1
u_vio_wrapper/vio_i/vio_0_probe_out2[3:0]	[H] 8		Output	hw_vio_1
u_vio_wrapper/vio_i/probe_in0_1[3:0]	[H] 8		Input	hw_vio_1
u_vio_wrapper/vio_i/probe_in1_0_1[3:0]	[H] 8		Input	hw_vio_1

(a) VIO

 

(b) FPGA - Led 4 prendido

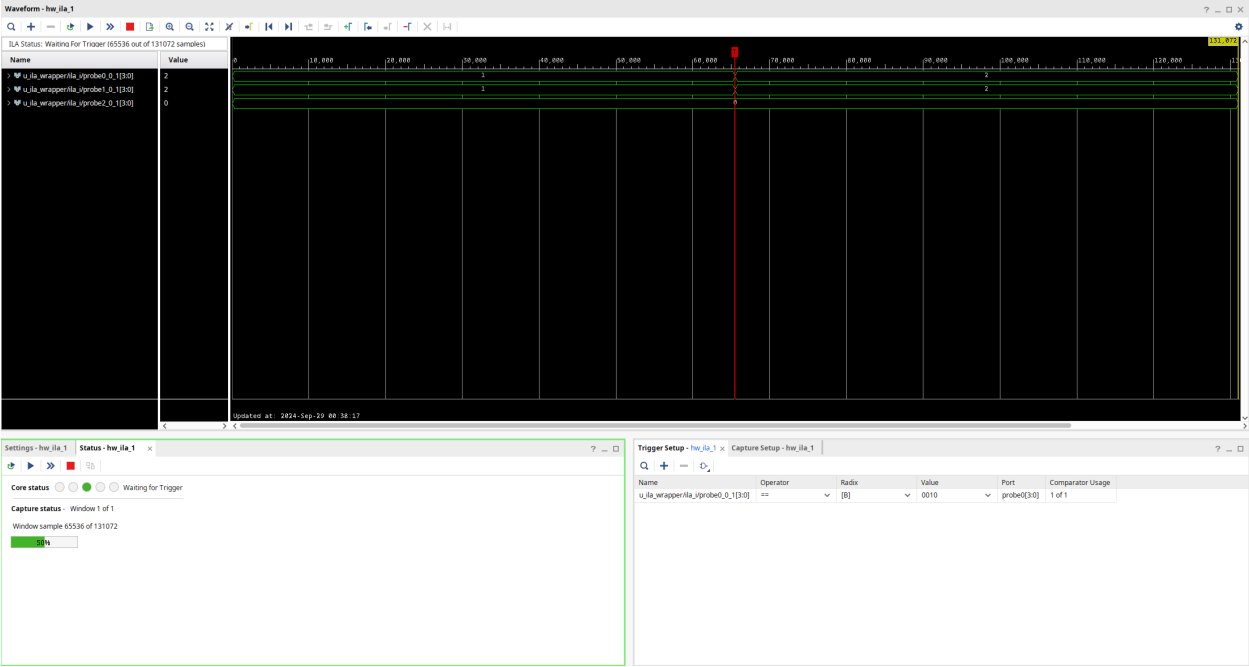

(c) ILA - Sampling constante en 50 %

Figura 6: Led quieto

 


Figura 7: FPGA en reset - Led 0 prendido